

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



GAYATRI VIDYA PARISHAD COLLEGE OF ENGINEERING FOR WOMEN
(AUTONOMOUS)

(Affiliated to Andhra University, Visakhapatnam)

B.Tech. - I Semester Regular Examinations, December / January – 2025

ELEMENTS OF ELECTRONICS ENGINEERING

(CSE-AI&ML)

1. All questions carry equal marks
2. Must answer all parts of the question at one place

Time: 3Hrs.

Max Marks: 70

UNIT-I

1. a. Explain the energy band diagrams of Intrinsic and extrinsic semiconductors [7M]
- b. Discuss the properties of Intrinsic and extrinsic semiconductors. [7M]

OR

2. a. Compare Conductor, Insulator and Semiconductor. [7M]
- b. Explain Drift and Diffusion currents with necessary equations. [7M]

UNIT-II

3. a. Discuss how a Zener diode is used as a voltage regulator? [7M]
- b. Explain the Volt-Ampere characteristics of a Tunnel diode with the help of necessary diagrams. [7M]

OR

4. a. Explain Efficiency and Ripple factor of Half Wave rectifier with necessary equations. [7M]
- b. Draw Full-Wave Bridge rectifier circuit and describe its operation. [7M]

UNIT-III

5. a. Compare CE, CB, and CC Bipolar Junction Transistor (BJT) configurations. [7M]
- b. Derive the expression for collector current in BJT CE configuration and draw its output characteristics. [7M]

OR

6. a. Explain the need for biasing a transistor. Outline the operation of collector to base bias. [7M]
- b. Derive the expression for operating point of a voltage divider bias circuit. [7M]

UNIT-IV

7. a. Draw and explain the operation of RC coupled amplifier. [7M]
- b. Construct the small signal equivalent circuit of CE amplifier and derive the expression for A_I , A_V , R_I and R_O . [7M]

OR

8. a. Discuss the application of transistor as an amplifier. [7M]
- b. Construct the small signal equivalent circuit of CB amplifier and derive the expression for A_I , A_V , R_I and R_O . [7M]

UNIT-V

9. a. With the help of diagrams, outline the construction details of N-Channel JFET. [7M]
- b. Draw and explain the transfer characteristics of N-Channel JFET. [7M]

OR

10. a. Explain the construction of Enhancement Mode MOSFET. [7M]
- b. Compare Enhancement mode and Depletion Mode MOSFETs. [7M]