

**GAYATRI VIDYA PARISHAD COLLEGE OF ENGINEERING FOR WOMEN****(Autonomous)**

(Affiliated to Andhra University, Visakhapatnam)

II B.Tech. - I Semester Regular Examinations, Nov – 2025**ANALOG AND DIGITAL CIRCUITS**

(EEE)

1. All questions carry equal marks
2. Must answer all parts of the question at one place

Time: 3Hrs.**Max Marks: 70****UNIT-I**

1. a. Explain the working of two-level diode clipper with neat circuit diagram
b. With neat diagram explain the working of transformer coupled transistor amplifier
- OR
2. a. Explain the working of negative clamper circuit. Draw the required waveforms
b. With the neat diagram explain the working of two-stage RC coupled amplifier

UNIT-II

3. a. With a neat block diagram explain the working of a voltage series feedback amplifier. Obtain the expression for gain, Input resistance and output resistance with feedback
b. With the help of a circuit diagram and associated wave forms describe the working of basic triangular square wave generator using op-amps.
- OR
4. a. Show that the bandwidth increases in negative feedback amplifiers.
b. What are the different types of feedback amplifiers? Give their equivalent circuits

UNIT-III

5. a. Convert $(A0F9.0EB)_{16}$ to decimal, binary, octal.
b. Simplify the following function using K-Map method
 $F(A,B,C,D) = \Sigma(0,1,2,3,4,6,9,10) + d(7,11,12,13,15)$
- OR
6. a. Describe the operations performed by the following logic circuits with an example:
(i) Full adder ii) Decoder (iii) Encoder.
b. Design the 8:1 MUX for the given Boolean Expression $f = \Sigma m(1,3,4,11,12,13,14,15)$.

UNIT-IV

7. a. With the block diagram, Truth table, describe the principle operation of edge triggered negative JK flip flop.
b. Draw the block diagram of 3-bit up counter & explain its operation with truth table.
- OR
8. a. Draw and explain the operation of the Master Slave SR flip-flops with block diagram.
b. With a neat diagram, explain the operation of bidirectional shift register.

UNIT-V

9. a. Explain the operation of binary weighted resistor DAC
b. Draw and explain the operation of sample and hold circuits
- OR
10. a. Draw and explain the functional diagram of the successive approximation ADC converter.
b. Explain the operation of 2-bit DAC using R-2R circuit.