

Subject code: 24EC11RC04 R-24 Date of Exam: 30-06-2025

Gayatri Vidya Parishad college of Engineering

For Women

(Affiliated to Andhra University, Visakhapatnam)

I B.Tech., -II Semester Regular Examinations, June/July-2025

Elements of Electronics Engineering

(Common to CSE & IT)

SCHEME OF EVALUATION

Q. No	Sub Q. No	Solution / Description	Marks
1	a	Differentiate between conductors, insulators and semiconductors based on energy bands <u>Ans:</u> Energy band diagram for conductors Energy band diagram for insulators Energy band diagram for semiconductors Explanation about conductors, insulators and semiconductors	7M 1M 1M 2M 3M
1	b	What is the total current in a semiconductor under both drift and diffusion mechanisms? <u>Ans:</u> Drift current definition and expression Diffusion current definition and expression Total current due to drift and diffusion in a semiconductor	7M 3M 3M 1M

Q.No	Sub Q.No	Solution/Description	Marks
2.	a.	Derive an expression for carrier concentration in intrinsic Semiconductors <u>Ans:</u> Statement of mass action law Intrinsic Semiconductor condition Mathematical relation of Intrinsic carrier concentration with temperature Simplified resultant expression	7m 1m 1m 4m 1m
2.	b.	How does conduction occur in conductors, Semiconductors, and insulators? <u>Ans:</u> conduction in conductors explanation conductivity in semiconductors Explanation about conduction in insulators	7m 2m 3m 2m
3.	a.	Sketch and explain the $V-I$ characteristics of a PN junction diode. <u>Ans:</u> $V-I$ characteristics of PN junction diode comparision between the characteristics of Silicon diode and germanium diode, its explanation	7m 3m 4m
3.	b.	Draw the circuit of a bridge rectifier without filter and explain its operation <u>Ans:</u> Bridge rectifier circuit diagram working operation Input and output waveforms	7m 2m 3m 2m

Q. No	Sub Q. No.	Solution / Description	Marks
4.	a.	Differentiate between transition capacitance and diffusion capacitance <u>Ans</u>: Transition capacitance definition, expression, explanation, diagram Diffusion capacitance diagram, definition, mathematical expression and its explanation (Or) Minimum 7 differences between the transition and diffusion capacitance	7m 3m 4m 7m
4.	b.	What is the role of a capacitor filter in a halfwave rectifier circuit with the help of circuit diagram? <u>As</u>: Half wave rectifier with capacitor filter circuit diagram Input and output waveforms Explanation about role of a capacitor filter, ripple factor expression	7M 2m 2m 3m
5.	a.	Draw the circuit and explain the operation of a BJT in CE configuration <u>As</u>: BJT in CE configuration circuit Input and output characteristics with explanation	7m 3m 4m

Q.No	Sub Q.No	Solution/Description	Marks
5.	b.	What are the three operating regions of a transistor? Explain each briefly <u>As</u>: Transistor operating regions and its applications (i) Saturation mode (ii) cutoff region (iii) Active region (iv) Inverse active region	7m 1m 6m
6.	a.	Analyze the input and output characteristics of a BJT in a CB configuration and discuss the effect of base width modulation. <u>Ans</u>:- BJT in CB configuration circuit diagram, its working operation Input characteristics } Output characteristics } Base width modulation effect	7m 3m 2m 2m
6.	b.	How do biasing techniques prevent thermal runaway? <u>Ans</u>: Thermal runaway explanation Biasing need in transistors Biasing techniques and prevent thermal runaway explanation	7m 3m 2m 2m

Q.No.	Sub Q.No	Solution/Description	Marks
7.	a.	Draw the circuit diagram of a two-stage Rc coupled amplifier and explain its working. <u>Ans</u> :: Two stage Rc coupled amplifier circuit diagram Explanation (working) Frequency response	7m 3m 3m 1m
7.	b.	Derive the expressions for voltage gain, current gain, input and output resistance of a CE amplifier using h-parameters. <u>Ans</u> :: CE amplifier h-parameter model circuit diagram Four parameters definition, final resultant expressions	7m 2m 5m
8.	a.	Explain the small signal model of a transistor using h-parameters <u>Ans</u> :: Two-port network model h-parameter model Four parameters with definition and its expressions	7m 1m 1m 5m

Q.No	Sub Q.No	Solution/Description	Marks
8	b.	Explain how gain changes in the low, mid and high-frequency ranges in a two-stage amplifier <u>As:</u> Frequency response graph Gain expression for two-stage amplifier Explanation about gain changes in (i) low frequency (ii) mid frequency (iii) high frequency	7m 1m 1m 5m
9	a.	Define and explain the JFET parameters. <u>As</u> Definition and mathematical expression for (i) Transconductance (ii) Input resistance (iii) Drain resistance (iv) Amplification factor & relation	7m 2m 1m 1m 3m
9	b.	Draw and explain the construction of n-channel Depletion MOSFET. <u>As</u> construction of n-channel MOSFET characteristics of MOSFET working operation	7m 2m 2m 3m

Q.No	Sub Q.No.	Solution / Description	Marks
10.	a.	Differentiate between Enhancement-mode and Depletion-mode MOSFETs	7M
		<u>Ans</u> : Minimum 7 differences between the Enhancement-mode and Depletion mode MOSFETs	7M
10.	b.	Draw and explain the transfer characteristics of N-channel JFET.	7M
		<u>Ans</u> :- Transfer characteristics waveform	2M
		Definition	1M
		Explanation about transfer characteristics of N-channel JFET	4M


 Dr Bpr Dilip
 Asst. professor
 ECE

Prepared by
 N. Roopa Vathi
 Asst. Professor
 ECE Department
 GVPCEW

