



Gayatri Vidya Parishad College of Engineering for Women
(Autonomous)
(Affiliated to Andhra University, Visakhapatnam)
 Madhurawada, Visakhapatnam

B.Tech. - I Semester Regular Examinations, December / January – 2025

Network Theory and Machines –(24EE11RC02)

Scheme of Valuation

Q No	Question
1(a)	Source transformation technique explanation ----- (2M) Source transformation technique explanation using an example ----- (1M) Explanation of Star to Delta transformation (formulas only) -----(2M) Explanation of Star to Delta transformation using an example -----(2M)
1 (b)	Obtaining equations by using suitable method (like mesh/nodal analysis/reduction technique etc.) -----(2M) Finding the responses: $i_1 = 3A, i_2 = 2A, i_3 = 1A$ -----(3M) $v_1 = 24V, v_2 = 6V, v_3 = 6V$ -----(2M)
2(a)	Explanation of nodal analysis -----(3M) Steps for applying nodal analysis -----(4M)
2(b)	Formation of three mesh equations Representation of current directions and voltage polarities of every element in the circuit diagram -----(1M) $18I_1 + 5I_2 + 3I_3 = 50$ -----(1M) $5I_1 + 9I_2 - 2I_3 = 10$ -----(1M) $3I_1 - 2I_2 + 5I_3 = 5$ -----(1M) Solving the above equations to find I_1, I_2, I_3 $I_1 = 3.29A$ -----(1M) $I_2 = -1.03A$ -----(1M) $I_3 = -1.39A$ -----(1M)
3(a)	Statement of Reciprocity theorem -----(3M) Verification of Reciprocity theorem using suitable example -----(4M)
3(b)	Equations of two port network representing transmission parameters -----(1M) Relevant circuit diagrams/method used for solving A,B,C & D parameters ----(2M) Finding parameters $A = 2.5, B = 4\Omega, C = 1S$ & $D = 2$ -----(4M)
4(a)	Finding Thevenin resistance $R_{th} = 9\Omega$ (with suitable circuit diagram) -----(2M) Finding Thevenin voltage $V_{th} = 22V$ (with suitable circuit diagram) -----(3M) Maximum power transfer $P_{max} = V_{th}^2 / (4 R_{th}) = 13.44W$ -----(2M)
4(b)	Finding Thevenin resistance $R_{th} = 4\Omega$ (with suitable circuit diagram) -----(1M) Finding Thevenin voltage $V_{th} = 30V$ (with suitable circuit diagram) -----(2M) Thevenin equivalent circuit -----(2M) Current through $R_L = 6\Omega$ is $3A$ -----(1M) Current through $R_L = 36\Omega$ is $3/4A$ or $0.75A$ -----(1M)
5(a)	Power factor definition -----(2M) Importance of Power factor -----(2M) Derivation of power factor expression for RL/RC/RLC circuit -----(3M)
5(b)	Circuit diagram -----(1M) Admittance calculation $Y = 0.015 - j 0.023 \text{ } \bar{\cup}$ or $0.028 \angle - 56.31 \bar{\cup}$ -----(3M) Current (I) = $1.54 - j2.31 A$ or $2.77 \angle - 53.31 A$ -----(3M)
6(a)	Circuit diagram -----(1M) Resonant frequency $f_0 = 50.33 \text{ Hz}$ (or) $\omega_0 = 316.23 \text{ rads/sec}$ -----(2M)

	Quality factor (Q) = 3.16 -----(2M) Band width (BW) = 100 rads/sec (or) 15.9 Hz -----(2M)
6(b)	Circuit diagram -----(1M) Phasor diagram representing relationship between input voltage and input current -----(2M) Power factor (P.f.) = 0.55 -----(2M) Apparent power (S) = 1110VA -----(1M) Active power (P) = 610.5 W -----(1M)
7(a)	Calculation of time constant (T) = 4 sec -----(2M) Finding initial conditions for $i_o(0^+) = -5A$ and $v_x(0^+) = 20V$ -----(2M) Solutions for $v_c(t) = 60 e^{-0.25t} V$ -----(1M) $v_x(t) = 20 e^{-0.25t} V$ -----(1M) $i_o(t) = -5 e^{-0.25t} A$ -----(1M)
7(b)	Initial condition $v(0) = 15V$ (with circuit diagram) -----(2M) Calculation of time constant (T) = 0.2 sec -----(2M) Expression for $v(t) = 15 e^{-5t} V$ -----(2M) Initial energy stored (W_o) = 2.25J -----(1M)
8(a)	Circuit diagram -----(1M) Voltage across capacitor at $t=0$ is 0V -----(2M) Voltage across capacitor at $t=\infty$ is 50V -----(2M) Calculation of time constant (T) = 0.05 sec -----(2M)
8(b)	Circuit diagram -----(1M) Finding initial conditions for i , $i(0) = 0A$ & $\frac{di(0)}{dt} = 1000 A/s$ -----(2M) Finding roots of characteristic equation, $s_{1,2} = -25 \pm j139.19$ -----(1M) Expression for $i(t) = 7.18e^{-25t} \sin(139.19t) A$ -----(3M)
9(a)	Equation of speed and different types of methods of speed control -----(1M) Explanation of each method with comparison between them, Armature voltage control method -----(2M) Armature resistance control method -----(2M) Field flux control method -----(2M)
9(b)	Operation principle of Transformer (statement only) -----(2M) Derivation of EMF expression ($E=4.44 \phi_m f N$) -----(5M)
10(a)	Constructional diagram with labelling -----(2M) Function of each part of DC machine ----- (5M)
10(b)	Double field revolving theory explanation with diagrams -----(5M) Significance of forward and backward rotating fields in the operation of single-phase induction motors -----(2M)

By
D Srinivas Reddy
Assistant Professor
EEE Department
GVPCEW